


A Sequentially Constructive Circuit Semantics for Esterel

Alexander Schulz-Rosengarten,
Reinhard von Hanxleden, Kiel University
and Michael Mandler, Bamberg University

Program Classes

Berry Constructive (BC) Esterel

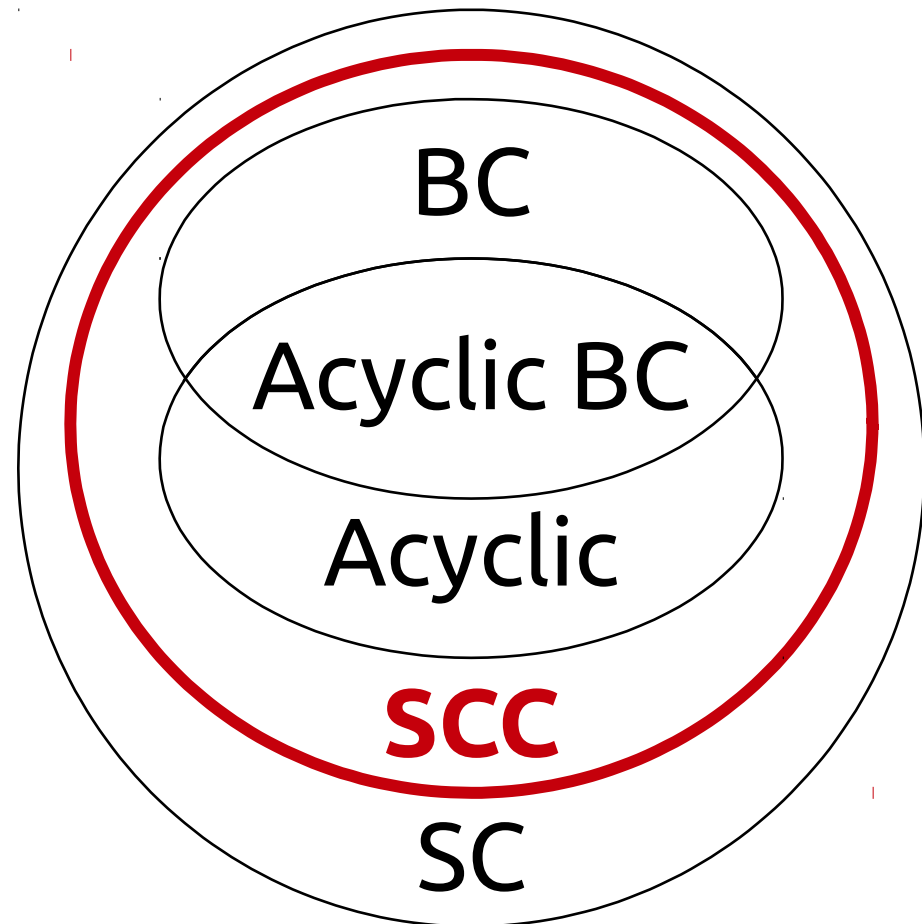- Circuit semantics
→ Delay insensitive
circuits



Sequentially Constructive Circuit (SCC) Semantics 2

Overview



Visibility



Visibility in circuits


emit S_0

Visibility on source level



Program Classes


module OffOn:

 



Esterel Constructive Circuits
 
```
module OffOn:  
  output S, T, U;  
  present S then emit T end;  
  emit S;  
  present S then emit U end
```





Esterel vs. Java / C / SCL

```
module OffOn:  
output S, T, U;  
present S then  
  emit T end;  
emit S;  
present S then  
  emit U end
```

```
bool S = T = U = false;  
if S {  
  T = true };  
S = true;  
if S {  
  U = true };
```

Signals encoded as booleans



Proposal

Constructive coherence law:

A signal is present/absent iff it must/cannot be emitted

Sequentially Constructive Coherence Law:


*A signal is present/absent iff it must/cannot be emitted
concurrently or sequentially preceding*


We say that an emit E is **SC-visible** to a present test P if:

- 1) E is concurrent to P or
- 2) E sequentially precedes P




SC-Visibility in Circuits

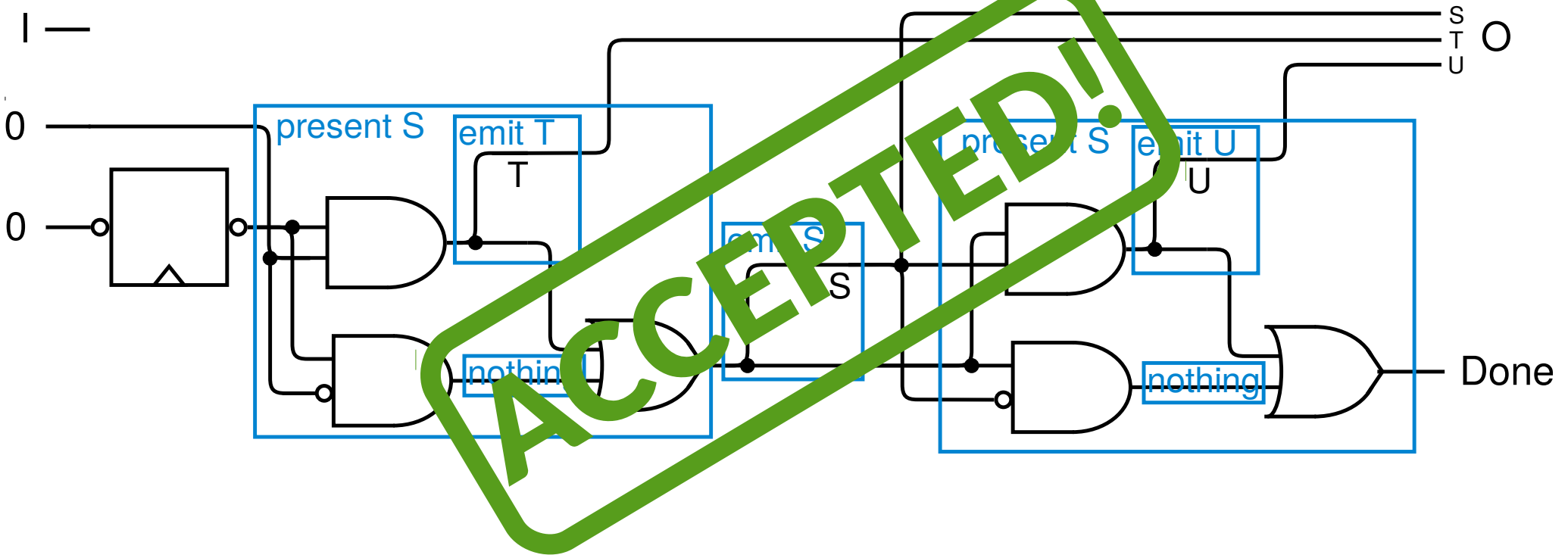

 


SCC Emit !s

 




SCC Present Test


s? P, Q

 

 

SCC Sequence


P; Q

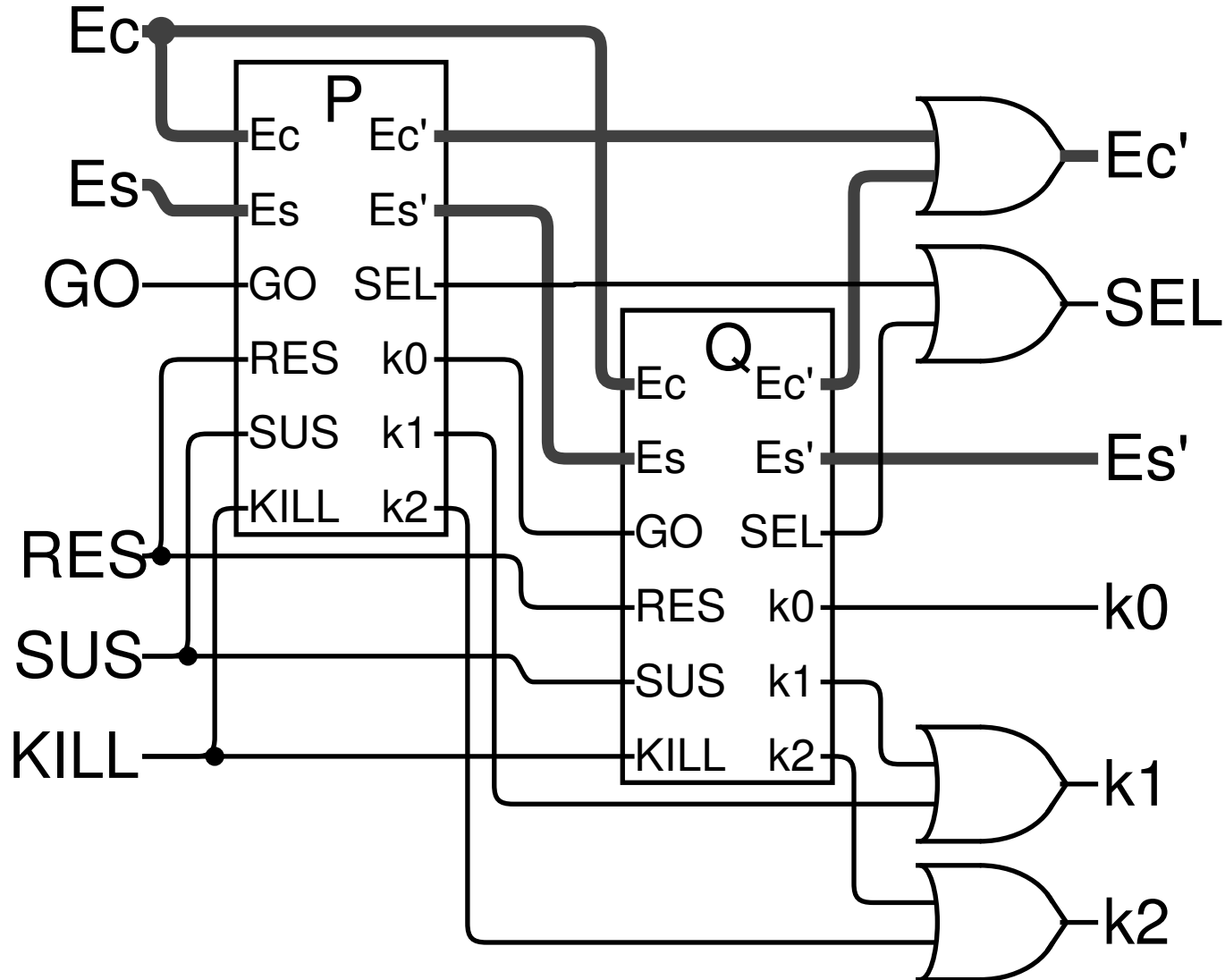



SCC Parallel


P || Q

 




Further SCC Rules


Signal

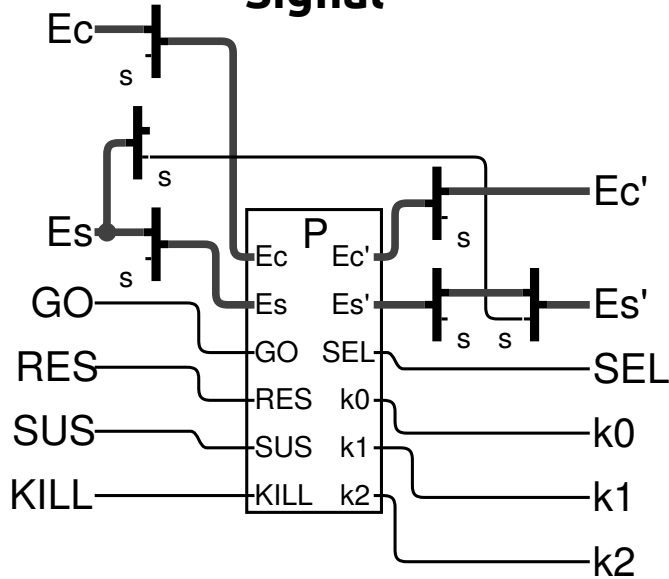


Loop

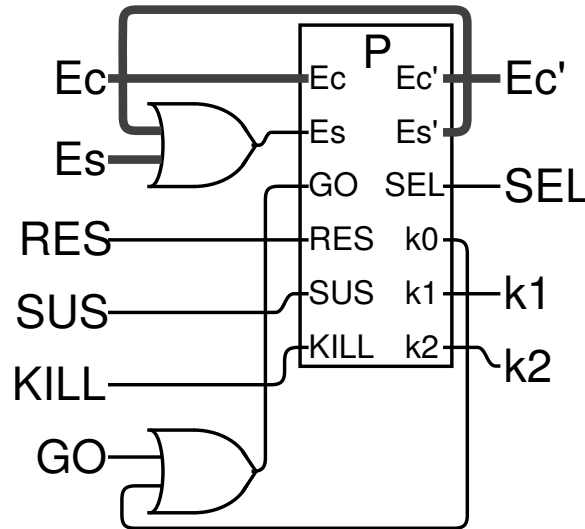


Pause

 


Exit

 


Nothing

 


Suspend

 


Trap

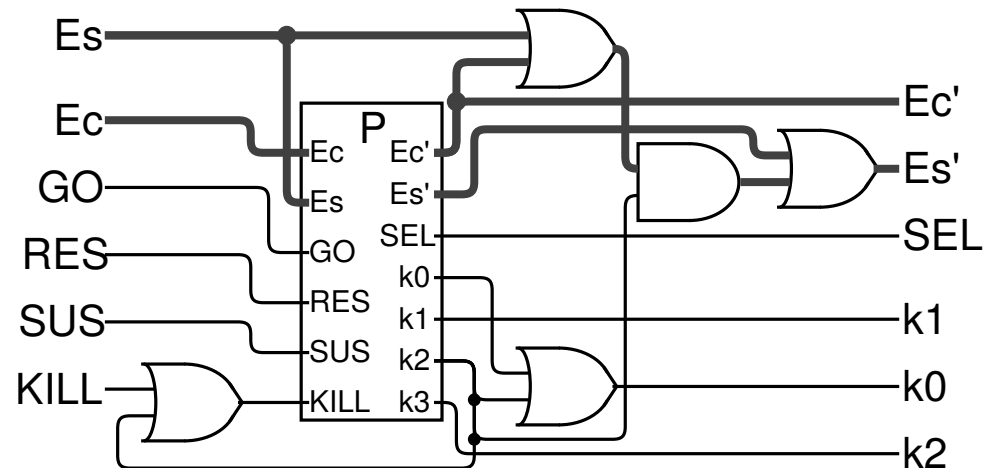

 

OffOn with SCC
 
```
module OffOn:  
  output S, T, U;  
  present S then emit T end;  
  emit S;  
  present S then emit U end
```




emit S₀

Back to Source Level

Applying SC-visibility to Esterel on source level.

Static Single Assignment Form
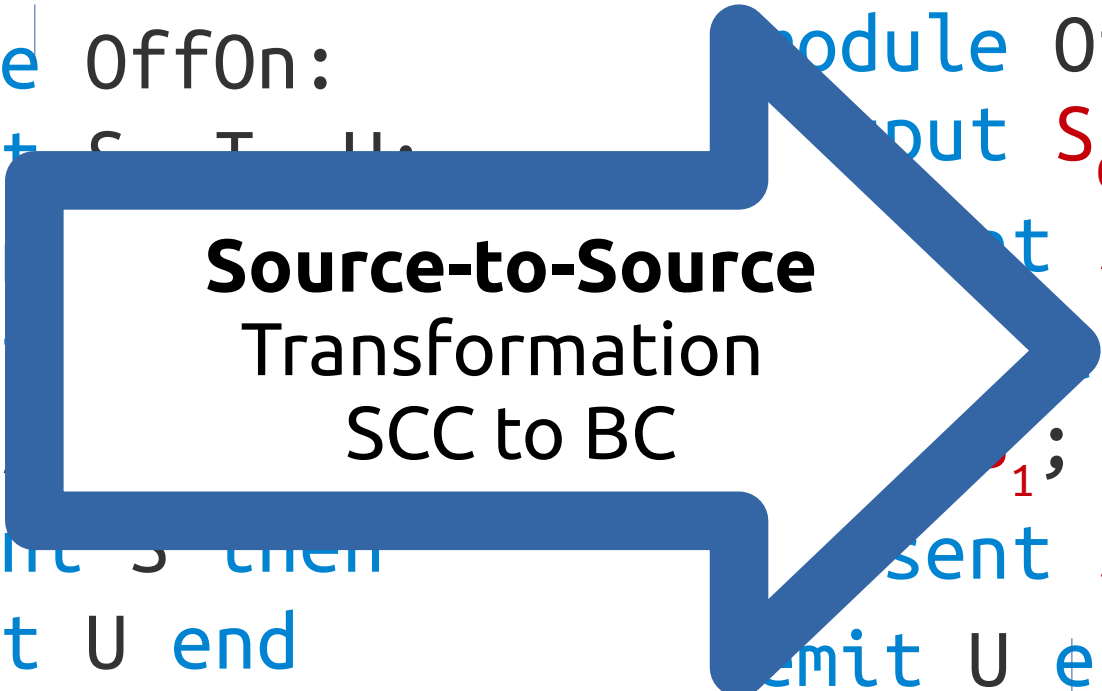
```
module OffOn:
output S, T, U;
present S then
  emit T;
end
emit U;
present U then
  emit S;
end
```




**Source-to-Source
Transformation
SCC to BC**

```
module OffOn:
output S0, S1, T, U;
present S0 then
  emit T;
end;
emit U;
present S1 then
  emit U;
end
```


emit S₀

Concurrent SSA for Esterel



```
module ST:  
output S, T;  
[  
  present S then  
    emit S end  
||  
  present T else  
    emit S end  
];  
present S then  
  emit T end
```

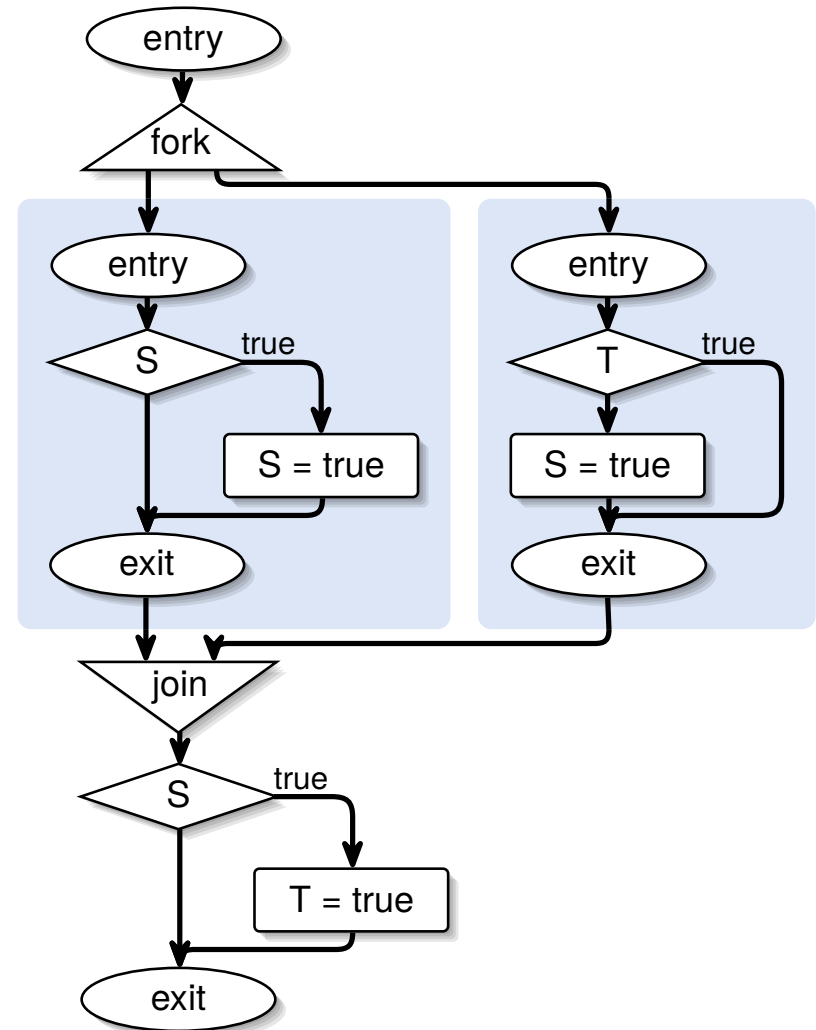



Concurrent SSA for Esterel

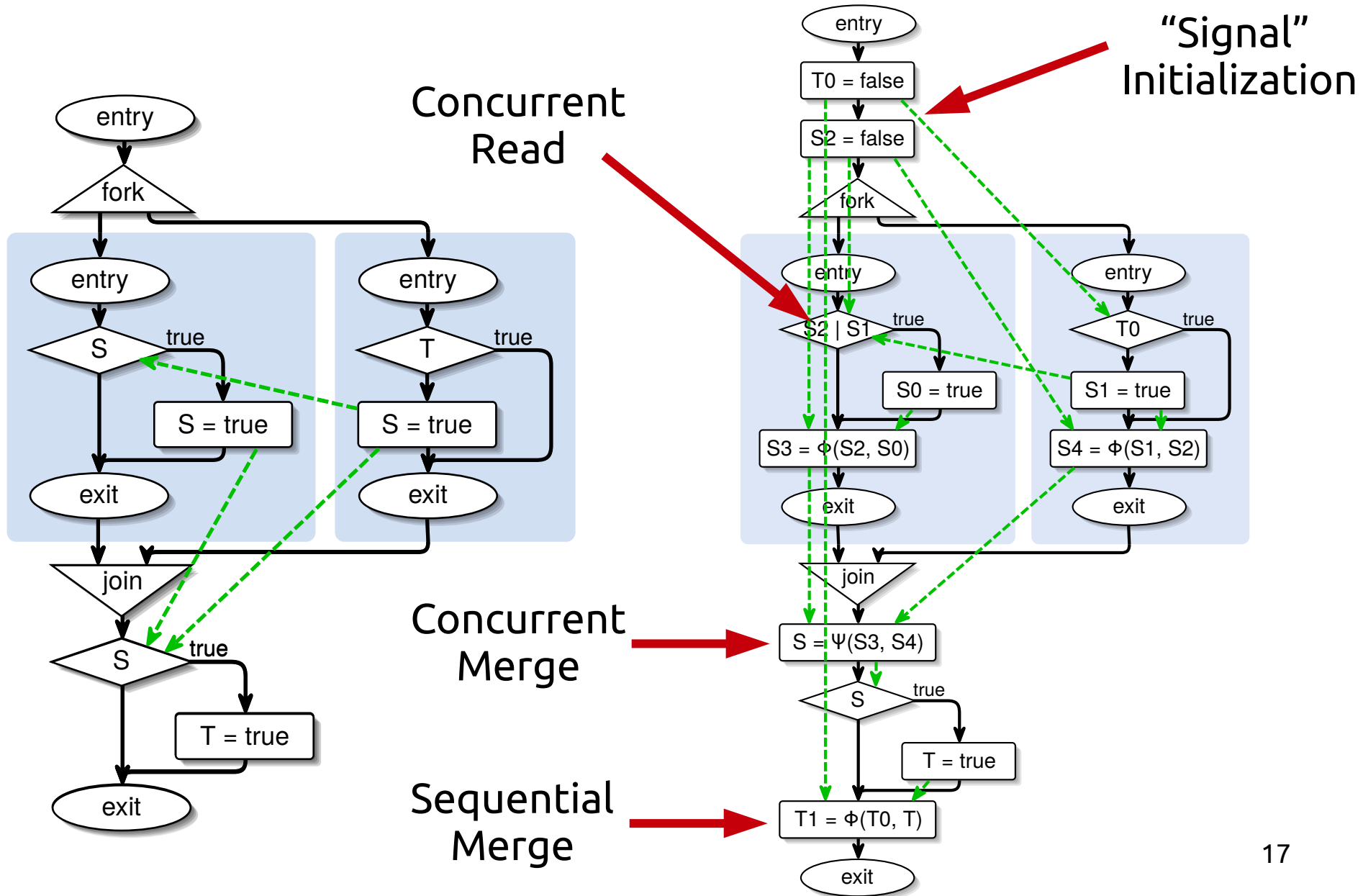

Concurrent SSA for Esterel

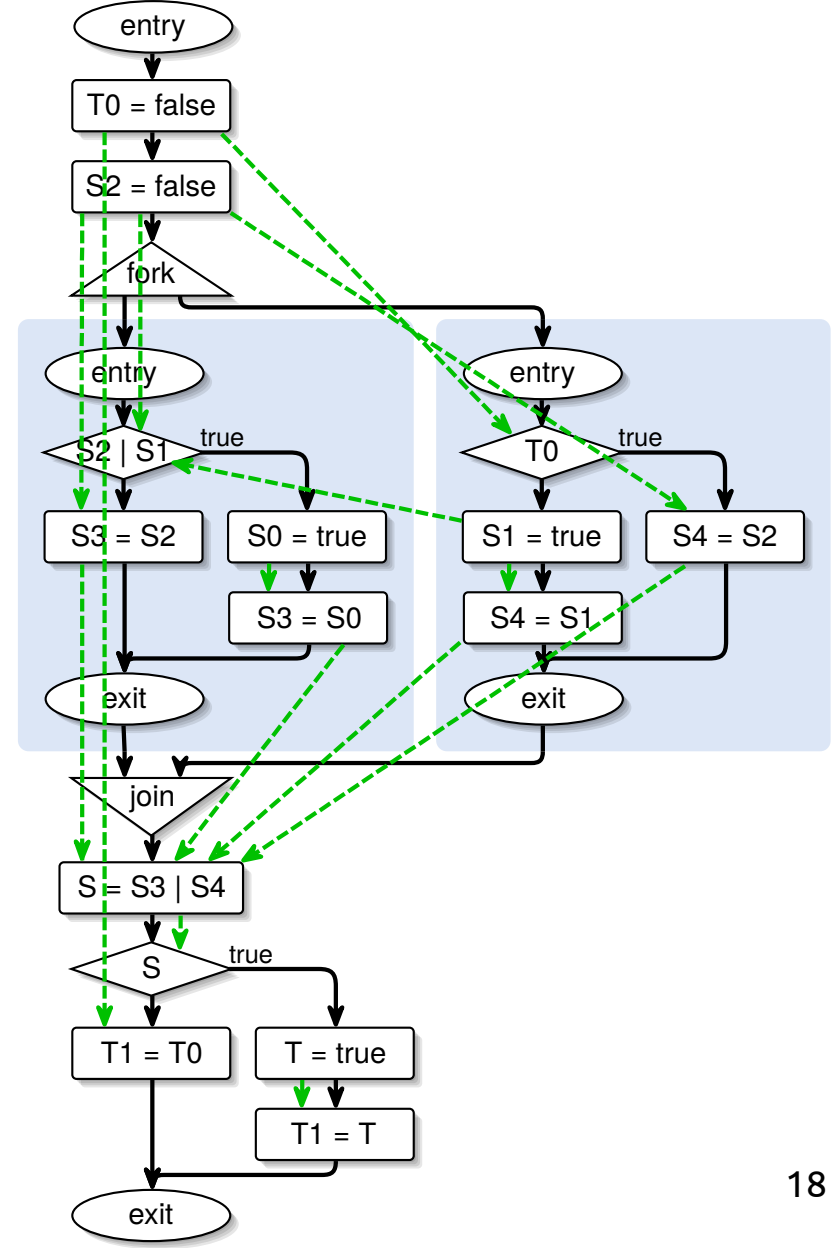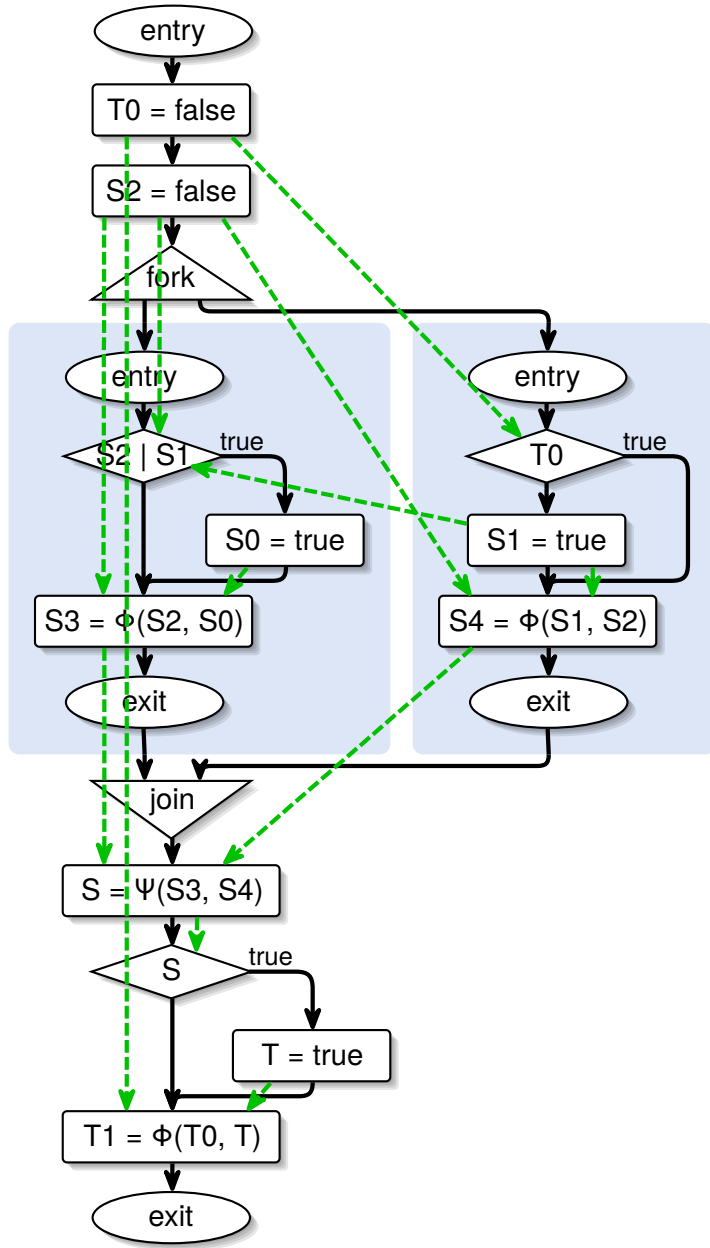


Concurrent SSA for Esterel

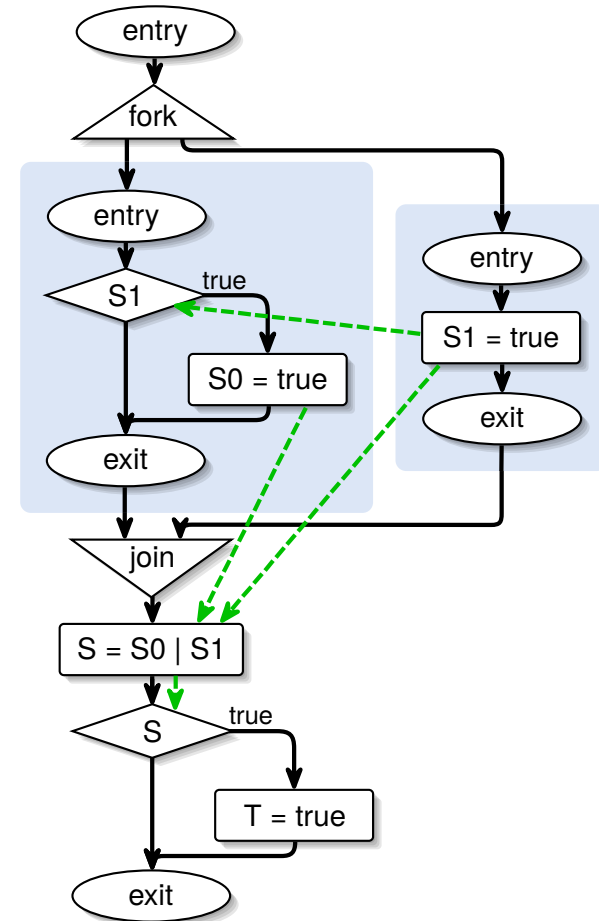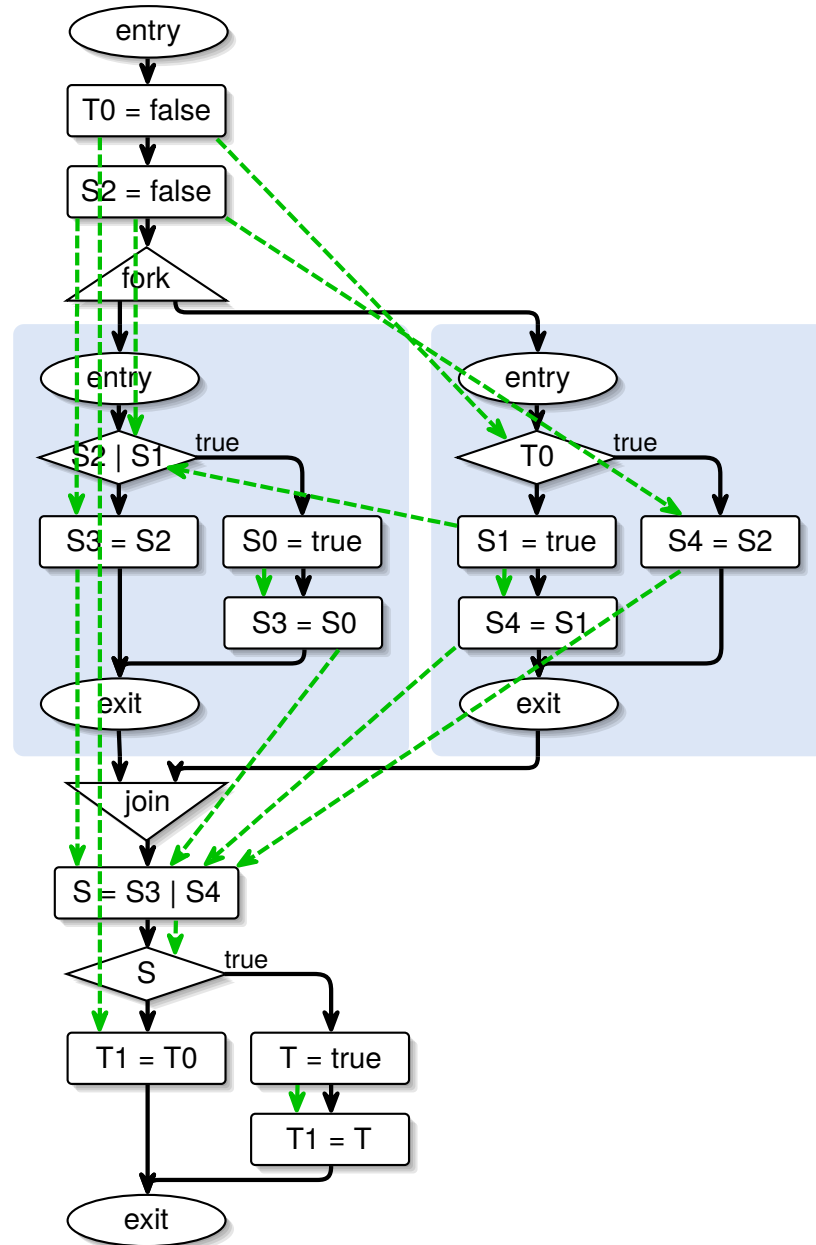

emit S₀

Concurrent SSA for Esterel

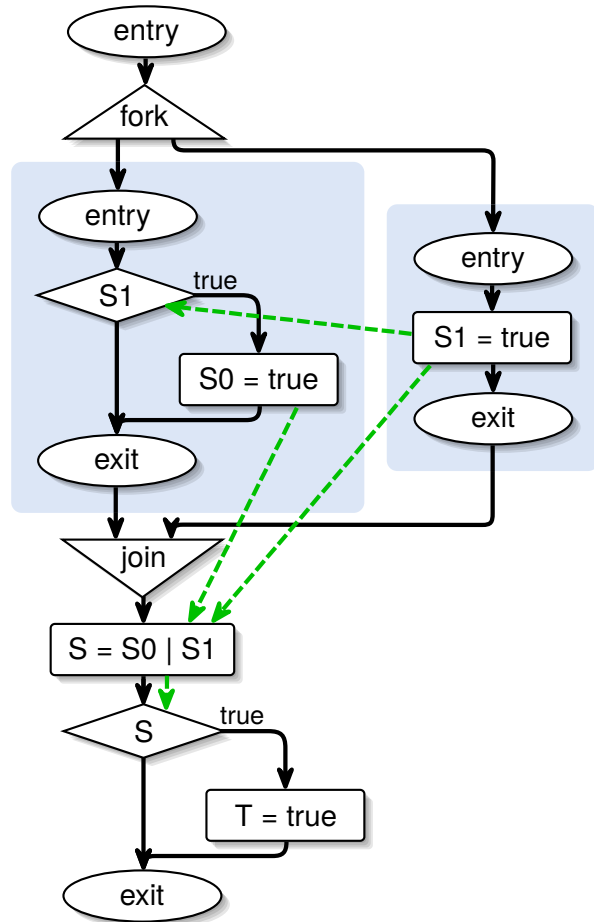

```
module ST-SSA:
output S, T;
signal S0, S1 in
[
  present S1 then
    emit S0 end
||
  emit S1
];
present S0 or S1 then
  emit S end;
present S then
  emit T end
```

Summary

- Sequentially Constructive Circuit (SCC) semantics for Esterel
- Source-to-source transformation from SCC programs into equivalent Berry constructive programs
- Claim conservativeness
 - $BC \Rightarrow SCC$
 - Preserving semantics
 - Proof sketch (WIP)

The End